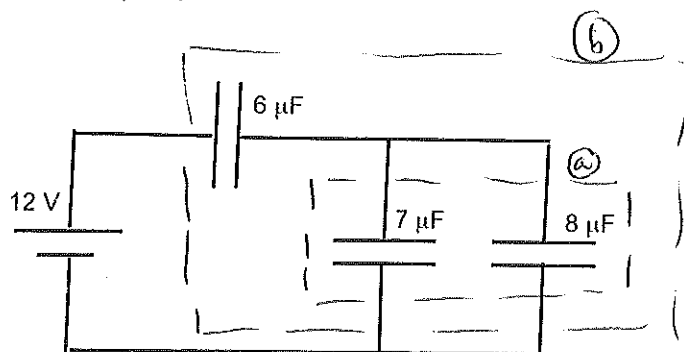


Name Solutions

ID _____



(4 points) For the circuit above, find the equivalent capacitance.

(a) $7\mu F \parallel 8\mu F \rightarrow 15\mu F$

(b) $15\mu F \text{ ser. } 6\mu F \rightarrow \frac{15 \times 6}{15 + 6} = \frac{90}{21} = \boxed{\frac{30}{7}\mu F}$

(2 points) What is the charge stored on the $6\mu F$ capacitor?

Total charge will appear on the $\pm$ plates of the series capacitor, so

$$Q = CV = \frac{30}{7}\mu F \times 12V = \boxed{\frac{360}{7}\mu C}$$


(4 points) What is the charge stored on the $7\mu F$ capacitor? the $8\mu F$ capacitor?

The voltage drop across each of these is the same, so using $Q = CV$, whatever V is (and it's not 12V!)

$$Q_7 = 7\mu \times V \rightarrow \frac{Q_7}{Q_8} = \frac{7}{8} \text{ so use } 15^{\text{th}}$$

$$Q_7 = \frac{7}{15} \times \frac{360}{7}\mu C = \frac{360}{15}\mu C = \boxed{24\mu C}$$

$$Q_8 = \frac{8}{15} \times \frac{360}{7} = \frac{8}{7} \times 24\mu C = \boxed{\frac{192}{7}\mu C}$$

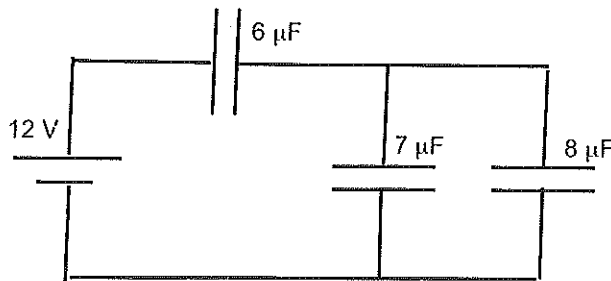Name Ratul IslamID 1448702

5/10

(4 points) For the circuit above, find the equivalent capacitance.

$$Q = CV$$

 C_{eq} for ||

$$C_{||} = 7 \mu F + 8 \mu F = 15 \mu F$$

 C_{eq} for series

$$\frac{1}{C_{eq}} = \frac{1}{6 \mu F} + \frac{1}{15 \mu F}$$

$$C_{eq} = \frac{C_1(C_2 + C_3)}{C_1 + C_2 + C_3}$$

$$C_{eq} = \frac{(6 \times 10^{-6} F)(15 \times 10^{-6} F)}{(6 + 15) \times 10^{-6} F}$$

$$(13 \times 10^{-6} F)$$

$$C_{eq} = 6.9 \times 10^{-6} F$$

(2 points) What is the charge stored on the 6 μF capacitor?
 Q on 6 $\mu F \rightarrow V_1$

$$Q = (C)(V) \quad (6.9 \times 10^{-6} F)(12 V) = 8.28 \times 10^{-5} \text{ F}\cdot V$$

(4 points) What is the charge stored on the 7 μF capacitor? the 8 μF capacitor?
 Q on 7 μF and 8 μF

$$Q \cdot 7 \mu F \parallel 8 \mu F \rightarrow V - V_1$$

$$\rightarrow Q_2 \rightarrow Q_3$$

$$Q = CV$$

for parallel
V is same

7 μF

$$Q = (12 V)(7 \times 10^{-6} F) = 8.4 \times 10^{-5}$$

$$Q = V(C_1 + C_2)$$

$$= 12 V(15 \times 10^{-6} F)$$


$$= 1.8 \times 10^{-4} \text{ F}\cdot V$$

8 μF


$$Q = (12 V)(8 \times 10^{-6} F) = 9.6 \times 10^{-5}$$

Name Reshu Sharma

ID _____

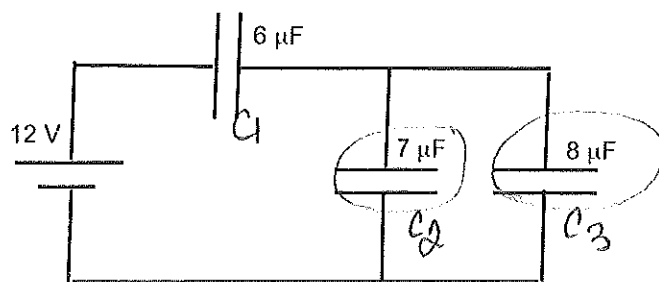

3/10

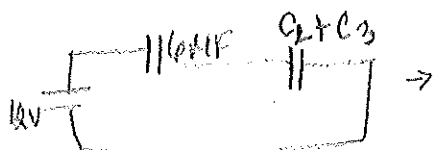(4 points) For the circuit above, find the equivalent capacitance, C_{eq} .

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2 + C_3}$$

$$C_{eq} = \frac{C_1 (C_2 + C_3)}{C_1 + C_2 + C_3} = \frac{6 \times 10^{-6} (7 + 8)}{6 + 7 + 8} = \frac{9 \times 10^{-11}}{2.1 \times 10^{-4}}$$

$$C_{eq} = 4.2 \times 10^{-7}$$

(2 points) What is the charge stored on the 6 μF capacitor?

$$Q = C_1 V \quad Q = (6 \times 10^{-6} \text{ F}) \cdot (12 \text{ V}) = 7.2 \times 10^{-5}$$

(4 points) What is the charge stored on the 7 μF capacitor? the 8 μF capacitor?

$$\frac{Q}{C} = CV$$

$$Q \text{ on } C_2 \text{ and } C_3 \rightarrow V_2 - V_1$$

$$Q = C_1 V$$



$$Q_{tot} = Q_2 + Q_3$$

$$Q_{tot} = C_1 V_1 + C_2 V_2 + C_3 V_3$$

$$V_1 = 12 \text{ V}$$

$$12 - \frac{(7.2 \times 10^{-5})}{(7 \times 10^{-6})} =$$
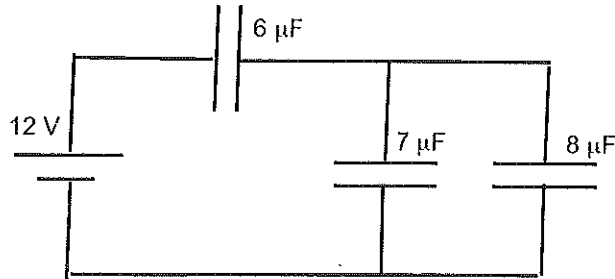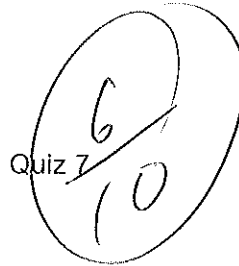
$$12 - \frac{(7.2 \times 10^{-5})}{(8 \times 10^{-6})} =$$



(4 points) For the circuit above, find the equivalent capacitance.

$$C_2 + C_3 = 15 \mu\text{F}$$

$$\frac{1}{C_{eq}} = \frac{1}{6 \mu\text{F}} + \frac{1}{15 \mu\text{F}} = \frac{21}{90} \mu\text{F}$$

$$C_{eq} = \frac{90}{21} \mu\text{F} = 4.28$$

$$C_{eq} = 4.28 \mu\text{F}$$

(2 points) What is the charge stored on the $6 \mu\text{F}$ capacitor?

$$Q = CV \quad V_i = \frac{Q}{C_i} \quad 12V = V_1 + (V_2 + V_3) \quad | \quad Q_1 = 51.4 \mu\text{C}$$

$$Q = 51.4$$

$$V_1 = \frac{51.4 \mu\text{C}}{6 \mu\text{F}} = 8.57 \text{ V}$$

(4 points) What is the charge stored on the $7 \mu\text{F}$ capacitor? the $8 \mu\text{F}$ capacitor?

$$Q = CV$$

$$V_2 + V_3 = 3.42 \quad V_{\text{rem}} = \frac{Q_{\text{rem}}}{C_{\text{rem}}}$$

$$Q_2 = CV_2$$

$$Q_3 = CV_3$$

$$V_2 = \frac{Q}{C}$$

$$V_3 = \frac{Q}{C}$$

$$(Q_2 + Q_3) = (V_2 + V_3)(C_2 + C_3)$$


$$Q = VC$$

$$Q_2 = (1.86)(7) = 13.02 \mu\text{C}$$

$$Q_3 = (1.86)(8) = 14.88 \mu\text{C}$$

$$Q_2 = 11.172 \mu\text{C}$$

$$Q_3 = 14.552 \mu\text{C}$$

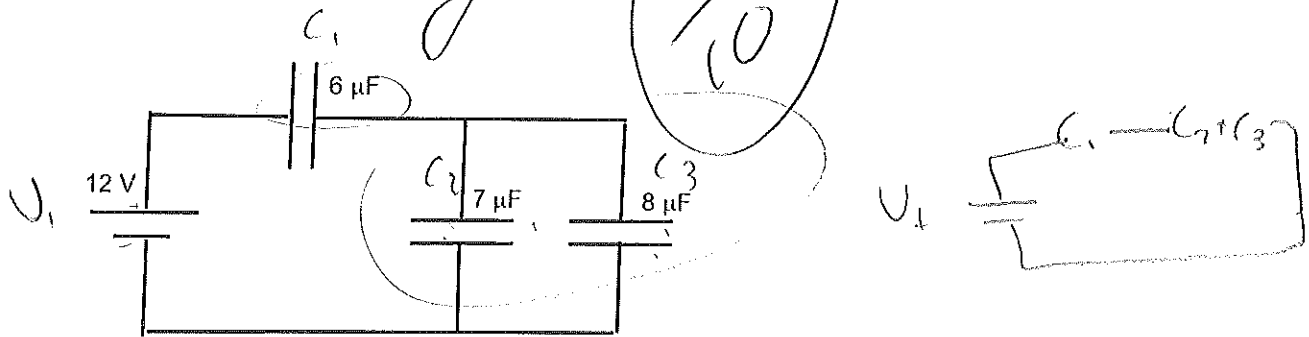Name Nicole RosneyID N15918363

(4 points) For the circuit above, find the equivalent capacitance.

$$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2 + C_3} \right)^{-1} = \left(\frac{1}{6 \times 10^{-6} \text{ F}} + \frac{1}{(7 \times 10^{-6}) + (8 \times 10^{-6})} \right)^{-1}$$

$$\boxed{4.3 \mu\text{F}}$$

$$Q = CV$$

$$V = \frac{Q}{C}$$

(2 points) What is the charge stored on the 6 μF capacitor?

$$Q_1 = C_1 V_1$$

$$V_1 + V_2 = V$$

$$Q_{tot} = C_{eq} V$$

$$V_1 = V - V_2$$

$$Q_{tot} = 5.16 \times 10^{-5} \text{ C}$$

$$V_1 = \frac{Q_{tot}}{C_{eq}} - \frac{Q_2}{C_2 + C_3}$$

$$\frac{5.16 \times 10^{-5}}{6 \times 10^{-6}} = 8.6$$

(4 points) What is the charge stored on the 7 μF capacitor? the 8 μF capacitor?

$$V_2 = V - V_1 = 12 - 8.6 = 3.4$$



$$Q_2 = (7 \times 10^{-6}) (3.4) = 2.4 \times 10^{-5} \text{ C}$$

$$Q_3 = (8 \times 10^{-6}) (3.4) = 2.7 \times 10^{-5} \text{ C}$$

Name FRANK AVEN

ID _____

8
10

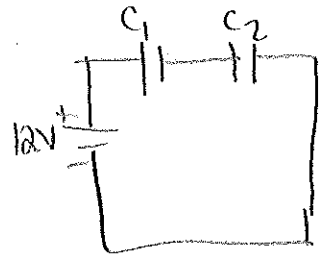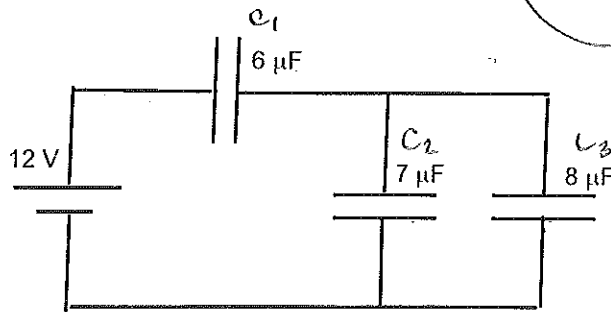

(4 points) For the circuit above, find the equivalent capacitance.

$$C_2 || C_3 = 15 \mu F$$

$$C_{eq} = C_1 + C_2 || C_3 = \frac{1}{6 \mu F} + \frac{1}{15 \mu F} = \underline{4.286 \mu F}$$

$$Q = CV$$

(2 points) What is the charge stored on the 6 μF capacitor?

$$Q = \frac{Q_{total}}{C_1} = \frac{51.432}{6} = 8.572$$

$$Q_{total} = (C_{eq})(V) = \underline{51.432}$$



$$Q_1 = C_1(V - V_1) = (6 \mu F)(12 - 3.4288) = 51.432$$

(4 points) What is the charge stored on the 7 μF capacitor? the 8 μF capacitor?

$$V_1 = \frac{Q_{total}}{C_1} = \frac{51.432}{15 \mu F} = 3.4288V$$

$$Q_{7\mu F} = (7 \mu F)(V - V_1) = (7 \mu F)(12 - 3.4288) = \underline{60}$$

$$Q_{8\mu F} = (8 \mu F)(V - V_1) = (8 \mu F)(12 - 3.4288) = \underline{68.576}$$

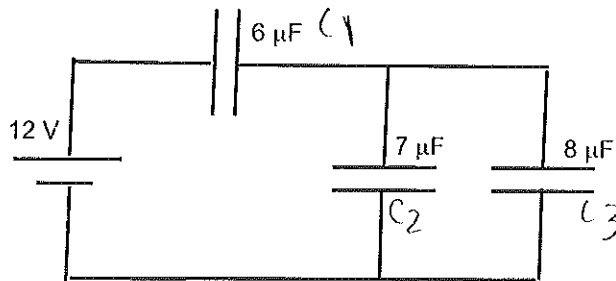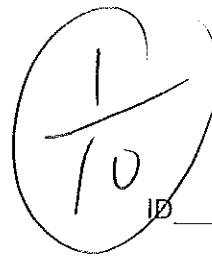Name Mari Kobakhidze

(4 points) For the circuit above, find the equivalent capacitance.

$$C_{(2+3)eq} = C_2 + C_3 = (7 + 8) \times 10^{-6} = 15 \times 10^{-6}$$

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_{2+3}}} = \frac{1}{\frac{1}{6 \times 10^{-6}} + \frac{1}{15 \times 10^{-6}}} = \frac{1}{0.167 \times 10^6 + 0.067 \times 10^6} = \frac{1}{0.234 \times 10^6} = 2.34 \times 10^{-5}$$

3

(2 points) What is the charge stored on the 6 μF capacitor?

$$Q = CV = 6 \times 10^{-6} \times 12 = 72 \times 10^{-6} = 7.2 \times 10^{-5}$$


-2

(4 points) What is the charge stored on the 7 μF capacitor? the 8 μF capacitor?

$$Q_2 = 12 \times 7 \times 10^{-6} = 84 \times 10^{-6} \quad Q_3 = 12 \times 8 \times 10^{-6} = 96 \times 10^{-6}$$

$$Q_2 = Q_3 = V(C_2 + C_3) = 12(7 \times 10^{-6} + 8 \times 10^{-6}) = 180 \times 10^{-6}$$

-4

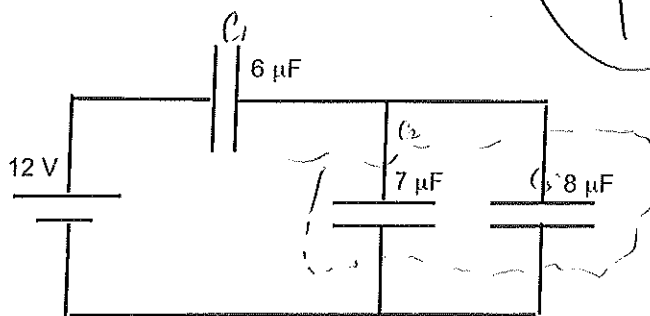Name Timothy ParboosinghD 0456235

$$C_{eq} = 7 \mu F + 8 \mu F$$

$C_2 + C_3$

$$C_{eq} = 15 \times 10^{-6} F$$

$C_2 + C_3$

(4 points) For the circuit above, find the equivalent capacitance.

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2 + C_3}$$

$$C_{eq} = \frac{C_1 (C_2 + C_3)}{C_1 + C_2 + C_3} = \frac{6 \times 10^{-6} (7 + 8)}{6 + 7 + 8} = 4.286 \times 10^{-6} F$$

$$\frac{1}{C_{eq}} = \left(\frac{1}{6 \times 10^{-6} F} + \frac{1}{15 \times 10^{-6} F} \right)$$

$$\frac{1}{C_{eq}} = 23333.33 F^{-1}$$

(2 points) What is the charge stored on the 6 μF capacitor?

$$Q_1 = C_1 V$$

$$Q_1 = 6 \times 10^{-6} (12V)$$

$$Q_1 = 7.2 \times 10^{-5} C$$

(4 points) What is the charge stored on the 7 μF capacitor? the 8 μF capacitor?

$$Q = V (C_2 + C_3)$$

$$Q = V (C_1 + C_2) \text{ "parallel rule"}$$

$$Q = 12V (7 \times 10^{-6} F + 8 \times 10^{-6} F)$$


$$Q = 12 \times (15 \times 10^{-6} F)$$

$$Q = 1.8 \times 10^{-4} C$$

$$V = V_1$$

Name Vincent Fung

ID _____

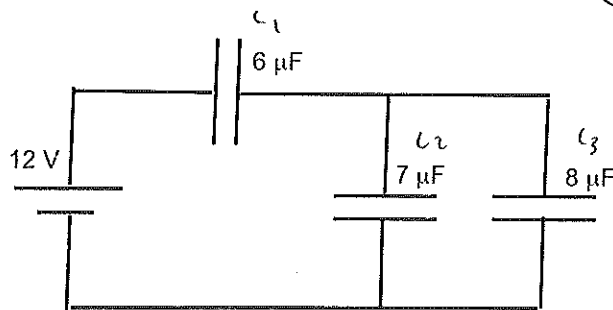

(4 points) For the circuit above, find the equivalent capacitance.

$$C_{eq} = \frac{C_1 (C_2 + C_3)}{C_1 + C_2 + C_3}$$

$$C_{eq} = C_1 + C_3$$

$$= \frac{6(7+8)}{6+7+8} = \frac{90}{21} \mu F$$

$$= 4.29 \mu F$$

$$7+8 = 15 \mu F$$

$$C_{eq} = 4.29 + 15 = 19.29 \mu F$$

(2 points) What is the charge stored on the 6 μF capacitor?

$$Q = CV \quad Q = C_{eq} V$$

$$Q = 4.29 (12) = 51.48 \mu C$$

$$(4.29 \times 10^{-6}) (12) = 51.48 \mu C$$

(4 points) What is the charge stored on the 7 μF capacitor? the 8 μF capacitor?

$$Q = CV \quad Q = C_{eq} V$$


$$Q_2 = Q_3 = 180 \mu C$$

$$(C_2 + C_3) (12) = 180 \mu C$$

/ 4

Name

Neo Meneze

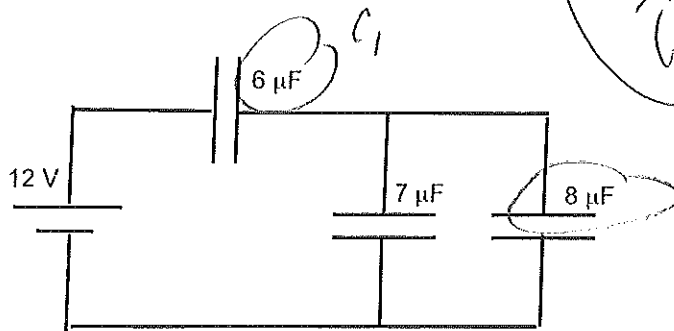

(4 points) For the circuit above, find the equivalent capacitance.

$$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2 + C_3} \right)^{-1} = \left(\frac{1}{6 \times 10^{-6} \text{ F}} + \frac{1}{7 \times 10^{-6} \text{ F} + 8 \times 10^{-6} \text{ F}} \right)^{-1}$$

$$C_{eq} = 4.3 \mu\text{F}$$

(2 points) What is the charge stored on the 6 μF capacitor?

$$Q \text{ on } C_1 \rightarrow V_1$$

$$\left(\frac{30}{7} \right) (12)$$

$$[5.1 \times 10^{-5} \text{ C}]$$

$$Q = C_1 V_1$$

$$(6 \mu\text{F}) (12) =$$

$$7.2 \times 10^{-5} \text{ F}$$

(4 points) What is the charge stored on the 7 μF capacitor? the 8 μF capacitor?

"11"
same
voltage.

$$Q = CV$$

$$Q \text{ on } C_2 \parallel C_3 \rightarrow V - V_1$$

$$Q_2, Q_3$$

$$V - V_1$$

$$= 12 - 8.575 = 3.425$$

$$8.57 \text{ V}$$

$$Q_2 = C_2 V_2$$

$$(7 \times 10^{-6}) (3)$$

$$[2.1 \times 10^{-5} \text{ C}]$$

$$Q_3 = C_3 V_3$$

$$(8 \times 10^{-6}) (3) =$$

$$[2.4 \times 10^{-5} \text{ C}]$$

$$Q = CV$$

$$\downarrow 15 \mu\text{F} (V)$$


$$5.14$$

$$3.425$$

Jimmy Jimmy Fuy

10/10

12998229

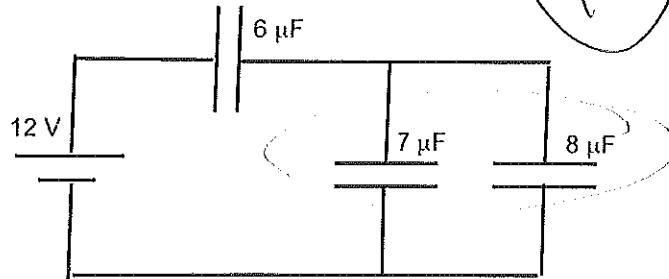

(4 points) For the circuit above, find the equivalent capacitance.

$$7118 \quad 7 + 8 \Rightarrow 15 \mu F$$

$$15 \mu F \text{ series } 6 \mu F \Rightarrow \frac{15 \cdot 6}{15 + 6} = \frac{90}{21} = \frac{30}{7} \approx 4.3 \mu F$$

(2 points) What is the charge stored on the $6 \mu F$ capacitor?

$$Q = C V_{\text{total}}$$

$$Q = (6 \mu F)(4.3)$$

$$Q = (6 \mu F)(12V) = 7.2 \times 10^{-5} F$$

$$Q = \left(\frac{30}{7} \mu F\right)(12V) \approx 5.1 \times 10^{-5} C$$

(4 points) What is the charge stored on the $7 \mu F$ capacitor? the $8 \mu F$ capacitor?

$$Q = CV$$

$$Q = \frac{30}{7} \cdot 12V = \frac{360}{7} \approx 51.43 C$$

$$V - V_1 \Rightarrow 12V - 8.57V = 3.43V$$

$$Q = CV$$

$$Q = 15 \mu F (V) = 5.1 \times 10^{-5} C$$

$$Q_{7\mu F} = 7 \mu F (3.43V) = 2.4 \times 10^{-5} C$$


$$Q_{8\mu F} = 8 \mu F (3.43V) = 2.7 \times 10^{-5} C$$

$$V_1 = \frac{Q}{C} = \frac{5.1 \times 10^{-5} C}{8 \mu F} = 8.57V$$


Name

Javinkhan

ID

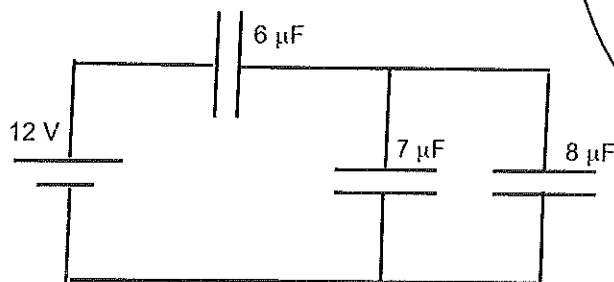

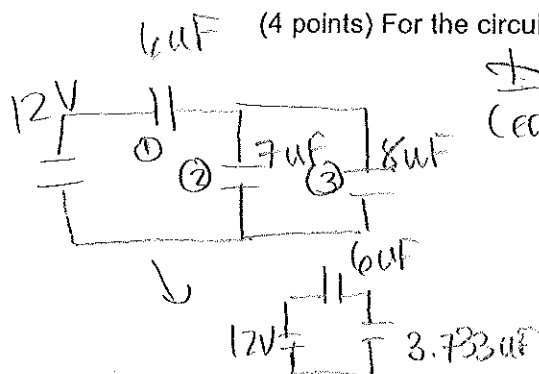(4 points) For the circuit above, find the equivalent capacitance.



$$C_{eq} = \frac{1}{\frac{1}{7 \mu F} + \frac{1}{8 \mu F}} = 0.267$$


$$C_{eq23} = 3.733 \mu F$$

$$C_{eq1} = 6 \mu F + 3.733 \mu F = 9.733 \mu F$$

(2 points) What is the charge stored on the $6 \mu F$ capacitor?

$$Q_1 = (6 \mu F)(12 V) = 72$$

$$Q = C_1 V_1$$

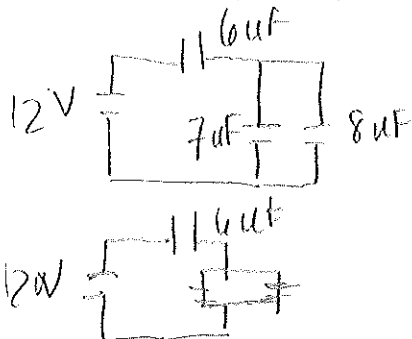(4 points) What is the charge stored on the $7 \mu F$ capacitor? the $8 \mu F$ capacitor?

$$Q = CV$$

$$Q_{TOT} = Q_1 + Q_{23}$$

$$Q_2 = Q_3 = Q_{23}$$


$$Q_{TOT} - Q_1 = Q_{23}$$

$$Q_{TOT} = C_{eq} V = (9.733 \mu F)(12 V) = 116.7996$$

$$Q_1 = C_1 V_1 = 72$$

$$Q_{23} = Q_{TOT} - Q_1 = 116.7996 - 72 = 44.7996$$

$$Q_2 = Q_3 = 44.7996 = Q_{23}$$

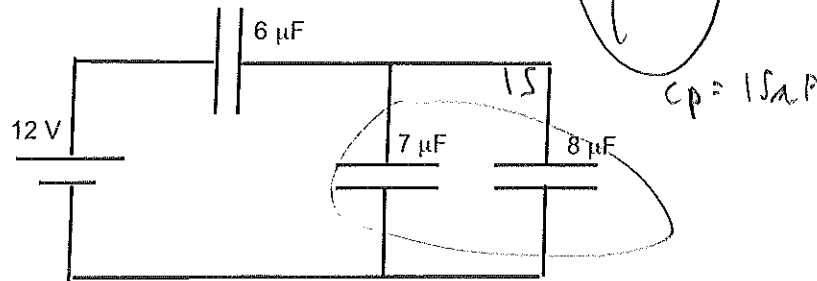Name Mahmoud DolahID 15363925

(4 points) For the circuit above, find the equivalent capacitance.



$$C_{eq} = \frac{(6 \mu F)(15 \mu F)}{6 \mu F + 15 \mu F}$$

$$C_{eq} = \frac{10}{21}$$

$$C_{eq} = 4.286 \mu F$$

(2 points) What is the charge stored on the 6 μF capacitor?

$$Q = CV$$

$$Q = (4.286 \mu F)(12V)$$

$$Q = 5.1429 \times 10^{-5}$$

charge is conserved
in series!

$$Q_{6 \mu F} = 5.1429 \times 10^{-5} C$$

$$Q = CV$$

$$V = Q/C$$

(4 points) What is the charge stored on the 7 μF capacitor? the 8 μF capacitor?

 V_p : Voltage on parallel part

$$12 - \frac{Q_{6 \mu F}}{6 \mu F} = V_p$$

$$12 - \frac{5.1429 \times 10^{-5}}{6 \times 10^{-6}} = \frac{24}{7} = V_p$$

Voltage is conserved
in parallel


$$Q = CV$$

$$Q_{7 \mu F} = (7 \mu F)\left(\frac{24}{7}\right)$$

$$Q_{7 \mu F} = 2.4 \times 10^{-5} C$$

$$Q_{8 \mu F} = (8 \mu F)\left(\frac{24}{7}\right)$$

$$Q_{8 \mu F} = 2.7429 \times 10^{-5} C$$

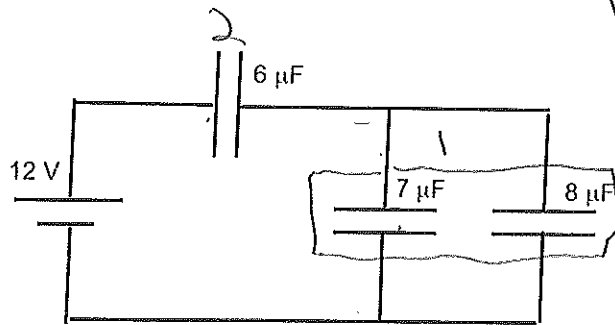Name Ryan JacobikID N10636708

(4 points) For the circuit above, find the equivalent capacitance.

~~$C_{eq} = \frac{1}{\frac{1}{7} + \frac{1}{8}} = \frac{56}{15}$~~
 ~~$C_{eq} = \frac{1}{\frac{1}{10} + \frac{1}{6}} = \frac{15}{4}$~~
 $C_{eq} = \frac{1}{\frac{1}{10} + \frac{1}{6}}$
 $C_{eq} = 15$
 $C_2 = 6$
 $C_{eq} = \frac{1}{\frac{1}{10} + \frac{1}{6}} = \frac{30}{7} \text{ or } 4.3 \mu F$

(2 points) What is the charge stored on the $6 \mu F$ capacitor?


$Q = CV$
 $Q = 4.3 \times 12$
 $Q_{total} = 51.6$
 $V = \frac{51.6}{6}$
 $V = 8.6 \text{ volts}$

(4 points) What is the charge stored on the $7 \mu F$ capacitor? the $8 \mu F$ capacitor?

~~$V = \frac{72}{6}$~~
 $V_1 = 8.6 \text{ volts}$

$V_2 = V - V_1 = 3.4$

$7 \mu F \quad Q = 23.8 = (3.4 \times 7)$
 $8 \mu F \quad Q = 27.2 = (3.4 \times 8)$

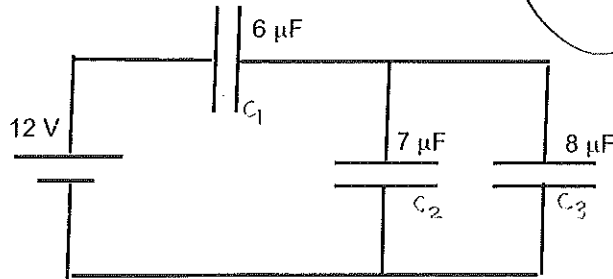Name Nauman ModyID NH227932

(4 points) For the circuit above, find the equivalent capacitance.

$$C_2 + C_3 = 7 + 8 = 15 \mu\text{F}$$

$$C_{\text{eq}} = \left(\frac{1}{C_1} + \frac{1}{C_2 + C_3} \right)^{-1}$$

$$= \left(\frac{1}{6 \times 10^{-6}} + \frac{1}{15 \times 10^{-6}} \right)^{-1}$$

$$C_{\text{eq}} = 4.3 \times 10^{-6} \text{ F} \approx 4.3 \mu\text{F}$$

(2 points) What is the charge stored on the $6 \mu\text{F}$ capacitor?

$$Q_1 = CV$$

$$= 4.3 \times 10^{-6} \times 12$$

$$= 5.14 \times 10^{-5} \text{ C} = 51.4 \mu\text{C}$$

(4 points) What is the charge stored on the $7 \mu\text{F}$ capacitor? the $8 \mu\text{F}$ capacitor?

$$Q = CV$$

$$V = \frac{Q}{C}$$

$$= \frac{51.4 \times 10^{-5}}{6 \times 10^{-6}}$$

$$= 8.57 \text{ V}$$


$$12 - 8.57 = 3.43 \text{ V}$$

$$Q_2 = 7 \times 10^{-6} \times 3.43$$

$$= 24 \mu\text{C}$$

$$Q_3 = 8 \times 10^{-6} \times 3.43$$

$$= 27 \mu\text{C}$$

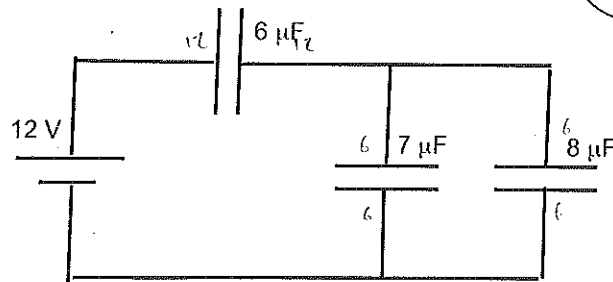Name Saha SalimID 

(4 points) For the circuit above, find the equivalent capacitance.

$$C_{eq} = \left[\frac{1}{C_1} + \frac{1}{C_2 + C_3} \right]^{-1}$$

$$= \left[\frac{1}{6 \mu F} + \frac{1}{15 \mu F} \right]^{-1}$$

$$C_{eq} = 4.29 \mu F$$

(2 points) What is the charge stored on the 6 μF capacitor?

$$Q_1 = C_1 V$$

$$= (6 \mu F)(12 V)$$

$$Q = 72 \mu C$$

(4 points) What is the charge stored on the 7 μF capacitor? the 8 μF capacitor?

$$Q_2 = C_2 V$$

$$= (7 \mu F)(12 V)$$

$$Q_2 = 84 \mu C$$

$$Q_3 = C_3 V$$

$$= (8 \mu F)(12 V)$$

$$Q_3 = 96 \mu C$$